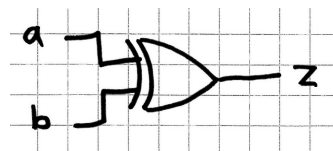


Digital Systems: Problem sheet 5


Mike Spivey, Trinity Term, 2022

1 An XOR gate $z = a \oplus b$ has the following truth table:

a	b	z
0	0	0
0	1	1
1	0	1
1	1	0



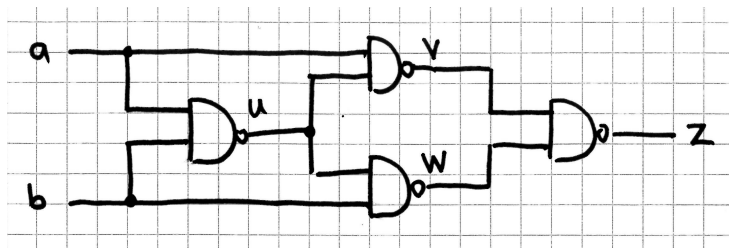- Show that \oplus is associative and commutative. Does it have an identity element?
- Show how to build an XOR gate from a 2-input OR gate, two 2-input AND gates and two inverters.
- Can you still build an XOR gate if one of the two AND gates is replaced by an OR gate?
- Show that the following circuit of four NAND gates also computes $z = a \oplus b$.



2 (a) Design a CMOS implementation of a NOR gate, with the following truth table.

a	b	z
0	0	1
0	1	0
1	0	0
1	1	0

2 Digital Systems: Problem sheet 5

- (b) In the lecture, we designed a CMOS gate that computed the function

$$z = \neg((a \wedge b) \vee c).$$

Design a gate that computes

$$w = \neg((a \vee b) \wedge c)$$

instead.


- (c) What general principle relates part (a) with the CMOS NAND gate designed in lectures, and part (b) with the AND-OR-NOT gate designed there?

- 3 (a) Design a *clocked set/reset latch* with the following behaviour. There are two inputs a and b ; if $a = 1$ at a clock edge, then the output z goes from 0 to 1. The output then remains at 1 until $b = 1$ at a clock edge, and then returns to 0. The behaviour if $a = b = 1$ at any clock edge can be whatever is easiest to implement.

- (b) Enhance your design to produce an additional output w that receives a pulse for exactly one clock cycle whenever the circuit is triggered by an event with $a = 1$, but does not receive another pulse until the circuit has been reset by setting $b = 1$ at a clock edge.

- 4 A T-type flip-flop has a control input t , in addition to an edge-triggered clock input. If $t = 1$ at a clock edge, then the flip-flop changes state; otherwise it remains in the same state.

q_t	t	q_{t+1}
0	0	0
0	1	1
1	0	1
1	1	0

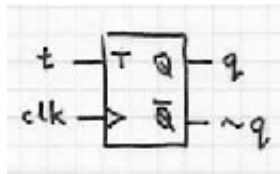

- (a) Show how to construct a T-type flip-flop from a D-type flip-flop and an XOR gate.
- (b) Show how to construct a synchronous binary counter from a row of T-type flip-flops and a row of AND gates. The counter should satisfy the specification $bin(a_{t+1}) \equiv bin(a_t) + 1 \pmod{2^n}$.
- (c) Show how to construct a synchronous binary counter from a row of D-type flip-flops and a row of half-adders.
- (d) Use your answer to part (a) to explain the connection between the circuit in parts (b) and (c).

- 5 Tests with an actual pull-cord light switch installed at the lecturer's home reveal that the light does not go on until the cord is released, but goes off as soon as it is pulled a second time. Modify the bathroom light-switch circuit to reproduce this behaviour.

- 6 In the lecture, it was shown that the set of connectives $\{\wedge, \vee, \neg\}$ is adequate to express any Boolean function, as is the singleton set $\{\text{NAND}\}$.

- (a) Show that the singleton $\{\text{NOR}\}$ is also adequate.

- (b) Show that the set $\{\text{XOR}, \neg\}$ is *not* adequate. *Hint: find a proper subset of the set of all Boolean functions of two variables x and y that contains x , y and the two Boolean constants and is closed under XOR and \neg .*

7 A *popcount circuit* has n Boolean inputs, and computes a binary number (with $\lfloor \log n \rfloor + 1$ bits) that counts the number of 1 bits among the inputs.

- (a) Show how to construct a popcount circuit from a balanced tree of adders so that the combinational path from each input bit passes through $O(\log n)$ adders before reaching the output.
- (b) If we use ripple-carry adders to implement the circuit, a k -bit adder has both size and worst-case delay that are linear in k . Use these facts to estimate the size and propagation delay of the popcount circuit.
- (c) In fact, some of the delays in ripple-carry adders are smaller than the estimate $O(k)$, because for $i \leq j$, the combinational path from the i 'th pair of inputs to the j 'th output has length proportional to $j - i + 1$. Use this fact to refine your estimate of the delay of the popcount circuit.

8 A bit-serial comparator has two inputs a and b . Successive binary digits of two numbers are presented at the two inputs on successive clock cycles, least significant bit first, and the circuit has two outputs L and G that indicate whether the number presented so far at a is less than or greater than the number presented at b (up to the preceding clock cycle); both outputs are zero if the numbers are equal so far. Thus, if the inputs at a are 0, 1, 1, 0 and those at b are 1, 0, 1, 1, then after 4 clock pulses the outputs are $L = 1$ and $G = 0$ because $6 = 0110_2$ is less than $13 = 1101_2$.

- (a) If the current outputs are L_i and G_i and the current input bits are a_i and b_i , show how to compute the next outputs L_{i+1} and G_{i+1} .
- (b) Use the previous part to give the design for a sequential circuit that inputs the numbers a and b and outputs L and G as described.
- (c) What would change if the numbers a and b were presented with their most significant bit first?