

Three instructions

Digital Systems – Lecture 23



UNIVERSITY OF
OXFORD

Department of
**COMPUTER
SCIENCE**


In this lecture

Using the datapath to implement three instructions.

- `adds r1, r2, r3`
- `str r0, [sp, #48]`
- `bgt .-4`

An ALU operation

adds r1, r2, r3

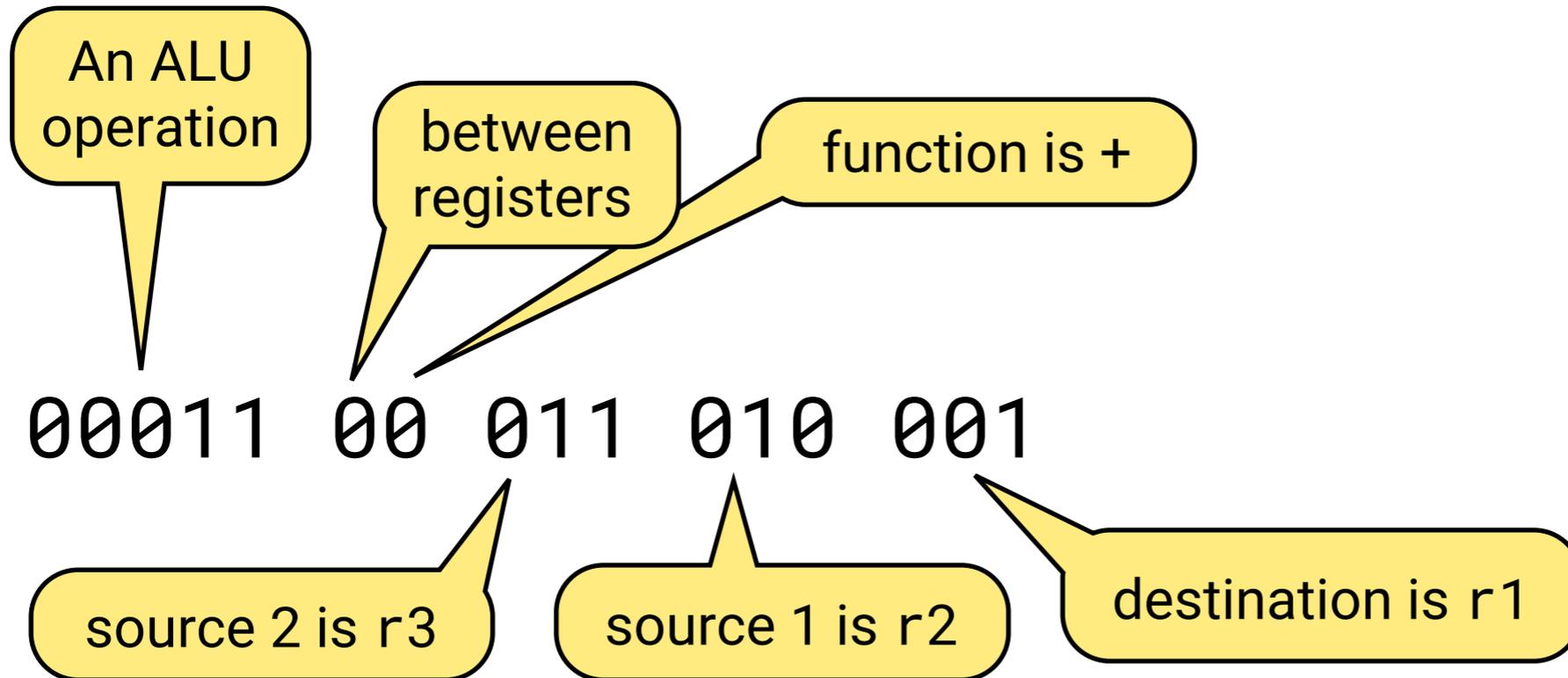

adds <Rx>, <Ry>, <Rz>


15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	0	0	1	1	0	0	Rz			Ry				Rx	

Rule 3 of 0 ... 31

	Instruction	cRegSel A/B/C	cRand2	cShiftOp/ Amt	cAlu Sel	cMem Rd/Wr	cWFlags/ Reg/Link
3 :	adds/subs	Ry/Rx/Rz					

- Use field Ry[3:5] to select the first register to be read.
- Use field Rz[6:8] to select the second register to be read.
- Use field Rx[0:2] to select the register to write.

Feeding the ALU

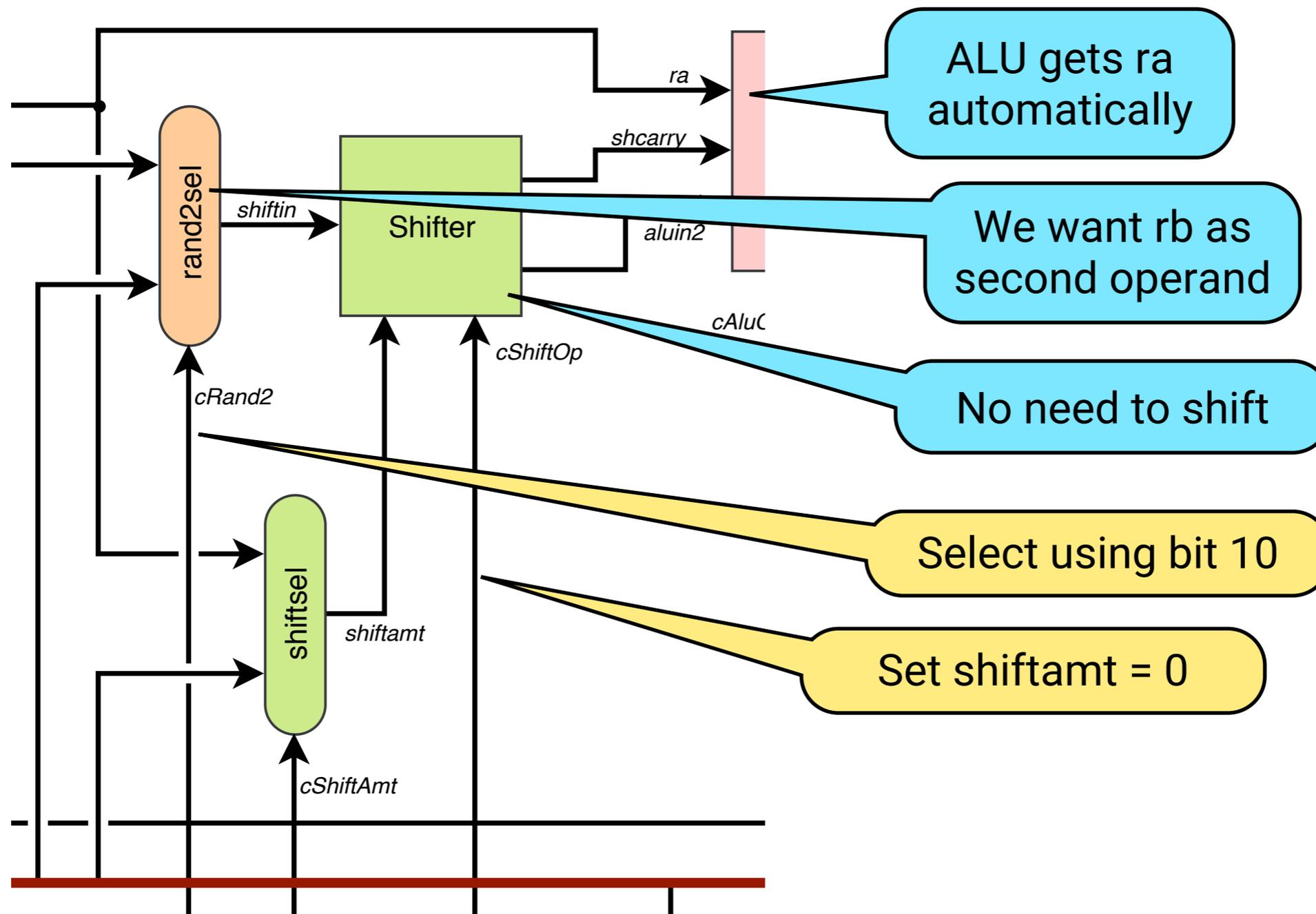


In the control word

	Instruction	cRegSel A/B/C	cRand2	cShiftOp/ Amt	cAlu Sel	cMem Rd/Wr	cWFlags/ Reg/Link
3 :	adds/subs	Ry/Rx/Rz	RImm3	Ls1/Sh0			

- Unusually, use bit 10 of the instruction to choose between rb and a 3-bit immediate.
- Shift the second operand (left) by 0 bits.

Performing the operation

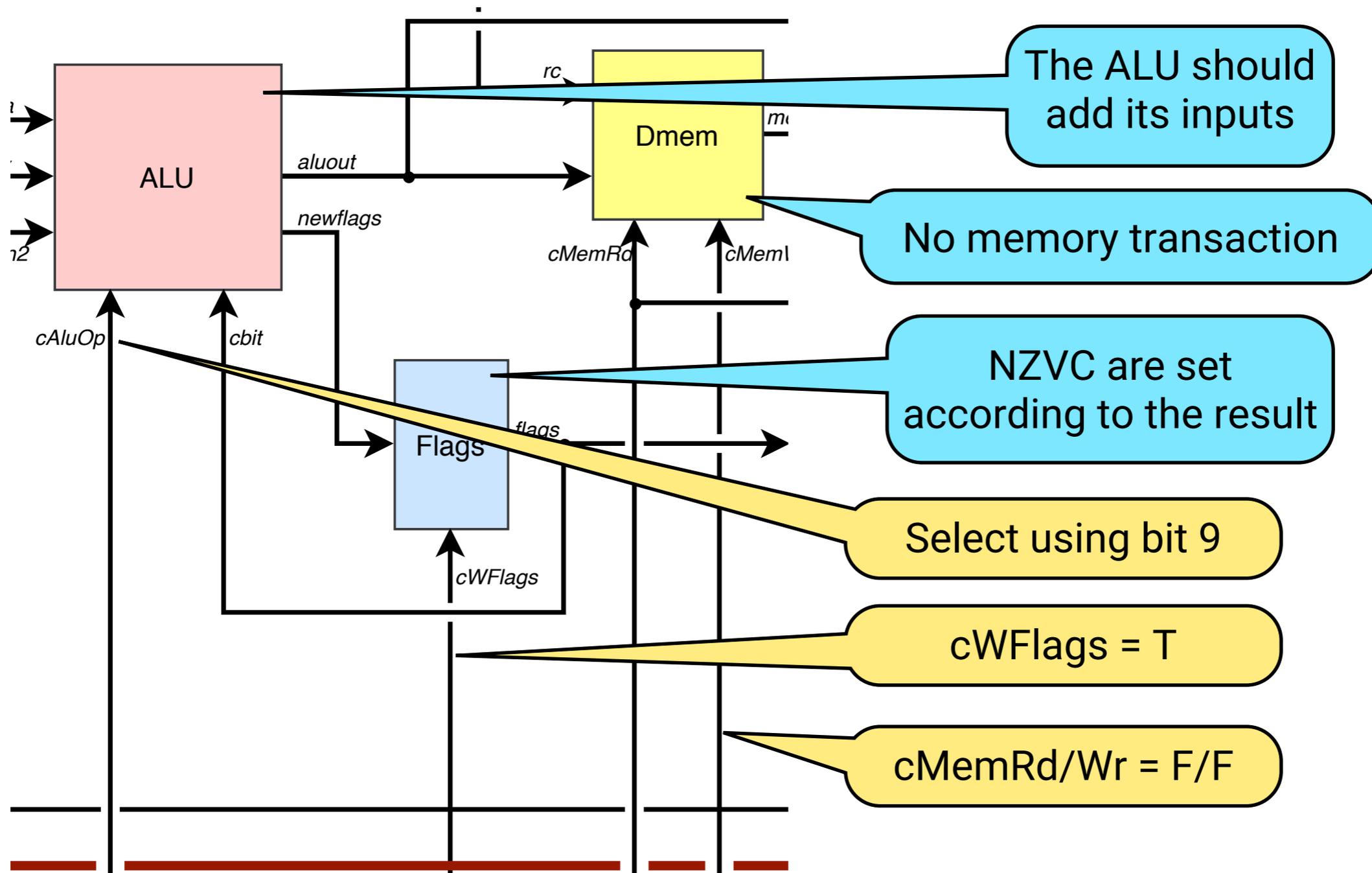


In the control word

	Instruction	cRegSel A/B/C	cRand2	cShiftOp/ Amt	cAlu Sel	cMem Rd/Wr	cWFlags/ Reg/Link
3 :	adds/subs	Ry/Rx/Rz	RImm3	Ls1/Sh0	Bit9	F/F	T/ /

- Unusually, use bit 10 of the instruction to choose between rb and a 3-bit immediate field.
- Shift the second operand (left) by 0 bits.

Writing the result

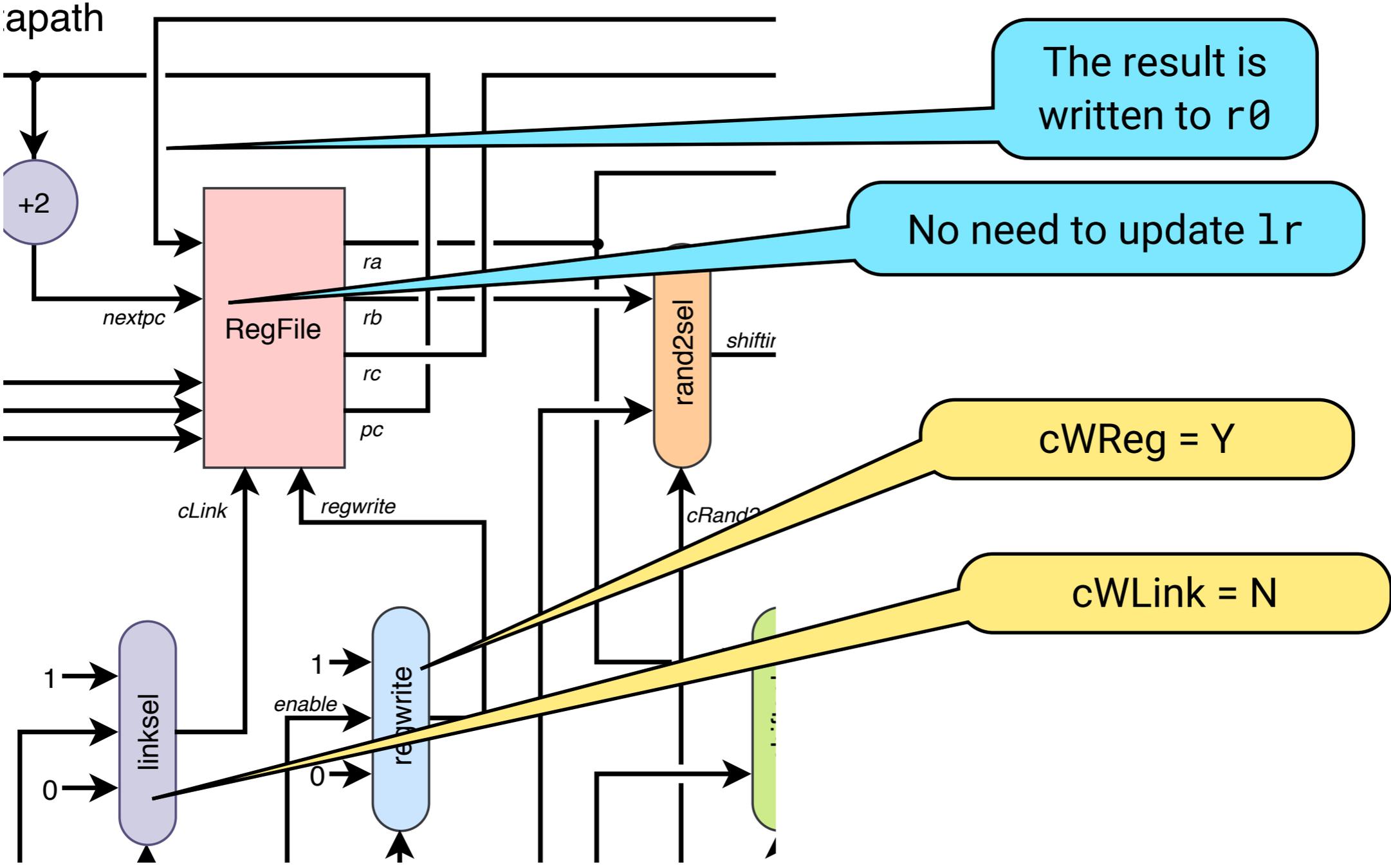

In the control word

	Instruction	cRegSel A/B/C	cRand2	cShiftOp/ Amt	cAlu Sel	cMem Rd/Wr	cWFlags/ Reg/Link
3 :	adds/subs	Ry/Rx/Rz	RImm3	Ls1/Sh0	Bit9	F/F	T/Y/N

- Write the result (from the ALU) into the third selected register.
- But don't write 1r with the address of the next instruction.

A store instruction

```
str r0, [sp, #48]
```


A special form of store

data from r0

10010 000 00001010

offset 4*12 from sp

```
str <Rw>,[sp,#<imm8>]
```

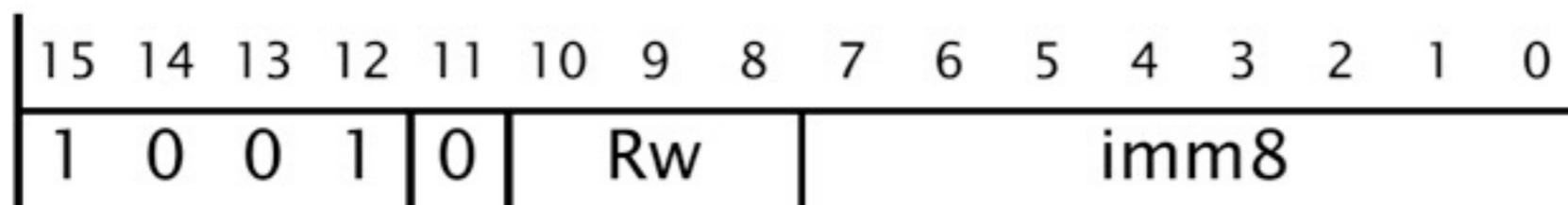


The plan

```
str r0, [sp, #48]
```

- Read registers `sp` and `r0`.
- Use the shifter and ALU to compute the effective address.
- Perform a write cycle with the data memory.

Selecting registers

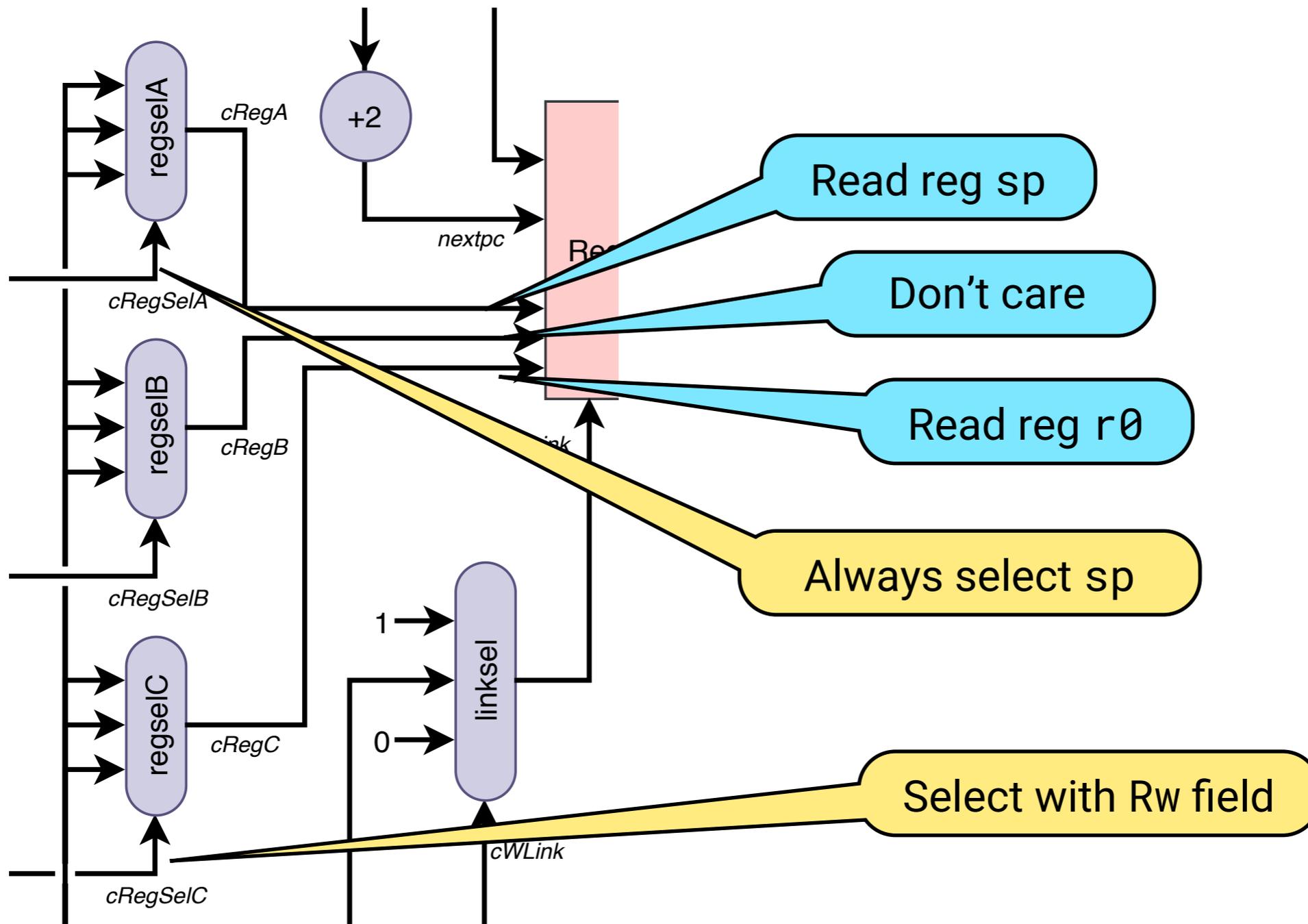


Rule 18 of 0 ... 31

	Instruction	cRegSel A/B/C	cRand2	cShiftOp/ Amt	cAlu Sel	cMem Rd/Wr	cWFlags/ Reg/Link
18:	str sp	Rsp/_/Rw					

- Always select sp as the first register to be read.
- Some register will be the second register, but we don't care which.
- Use field Rw[8:10] to select the third register to read.

Feeding the ALU

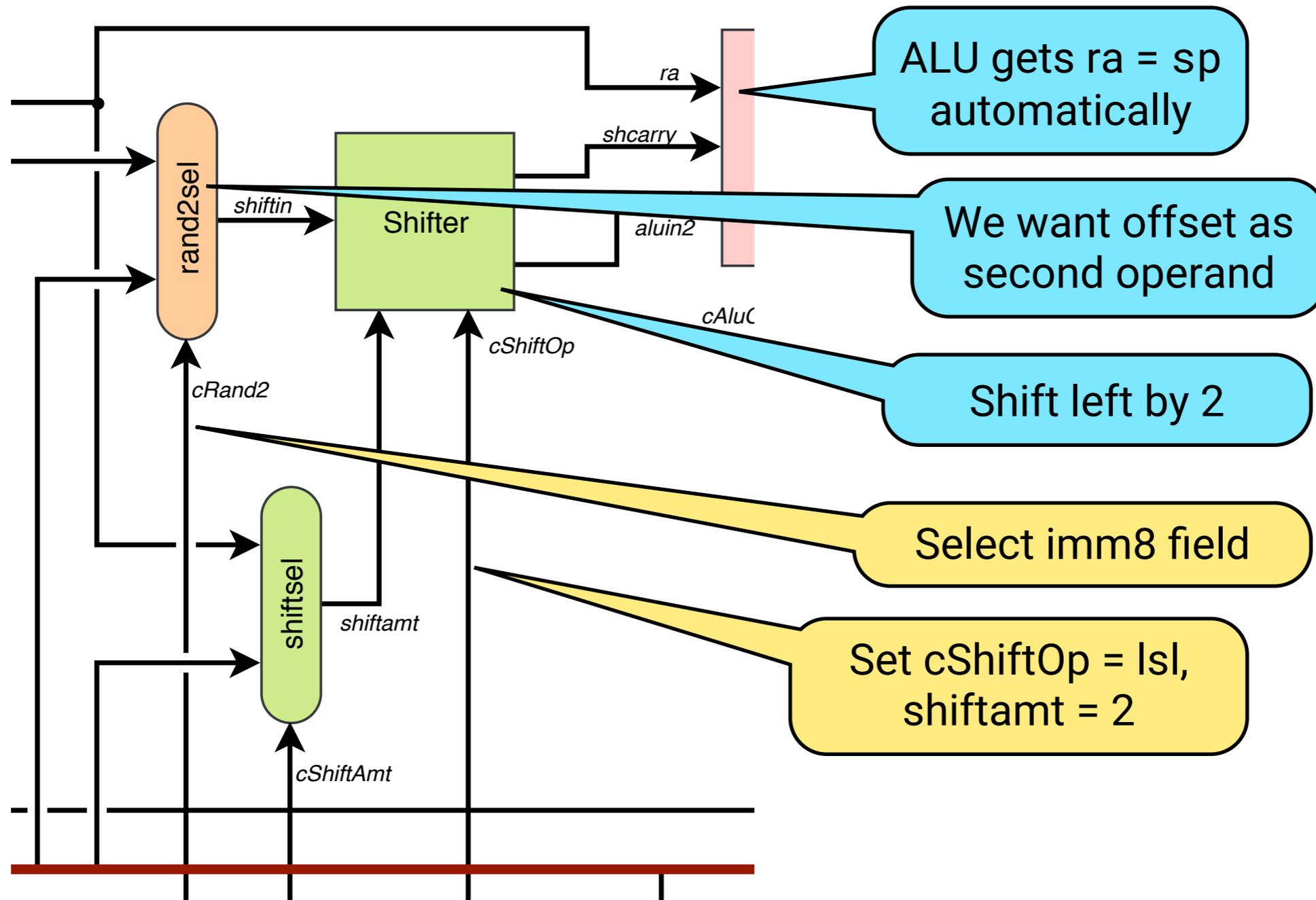


In the control word

	Instruction	cRegSel A/B/C	cRand2	cShiftOp/ Amt	cAlu Sel	cMem Rd/Wr	cWFlags/ Reg/Link
18:	str sp	Rsp/_/Rw	Imm8	Ls1/Sh2			

- The second ALU input comes from an immediate field.
- The value is scaled by 4, shifting left a constant 2 places.

Performing the operation

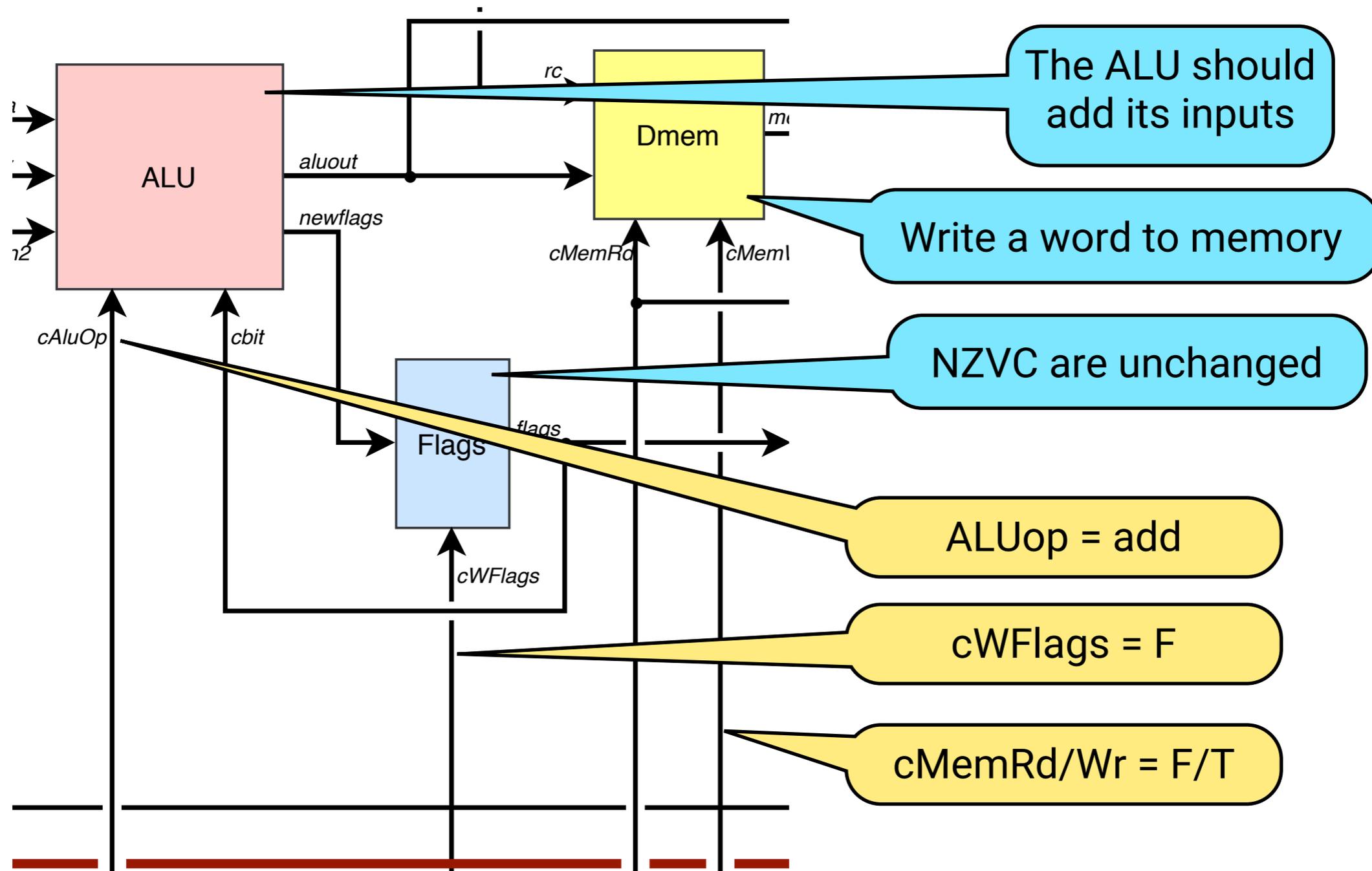

In the control word

	Instruction	cRegSel A/B/C	cRand2	cShiftOp/ Amt	cAlu Sel	cMem Rd/Wr	cWFlags/ Reg/Link
18:	str sp	Rsp/_/Rw	Imm8	Ls1/Sh2	Add	F/T	F/N/N

- The ALU adds `sp` and scaled offset to form the effective address.
- The value from the third register is written to that memory word.
- The flags are unchanged, no result is written to a register, and `1r` is not written.

A conditonal branch

bgt . -4

Conditonal branch


if greater than

```
label:  
  sub r0, r0, #1  
  cmp r0, #100  
  bgt label
```

1101 1100 11111100

offset $4 * (-4)$
relative to pc+4


b(c) <imm8>

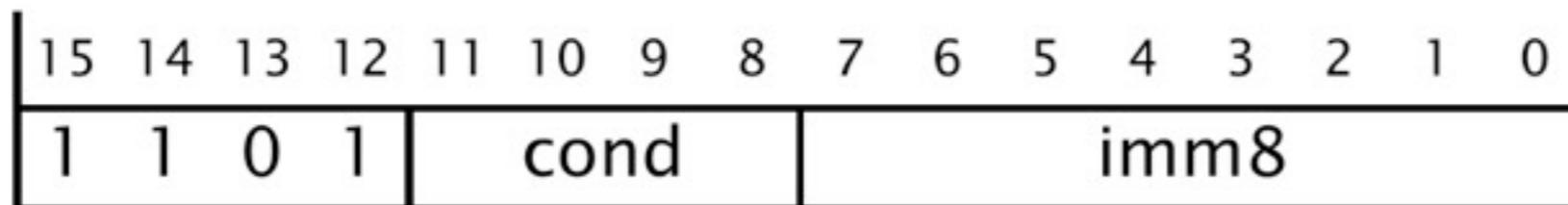

The plan

- Use the ALU to compute the branch target address, whether needed or not.
- Use the conditional execution unit to write back the result into the pc only if the branch is taken.

Selecting registers

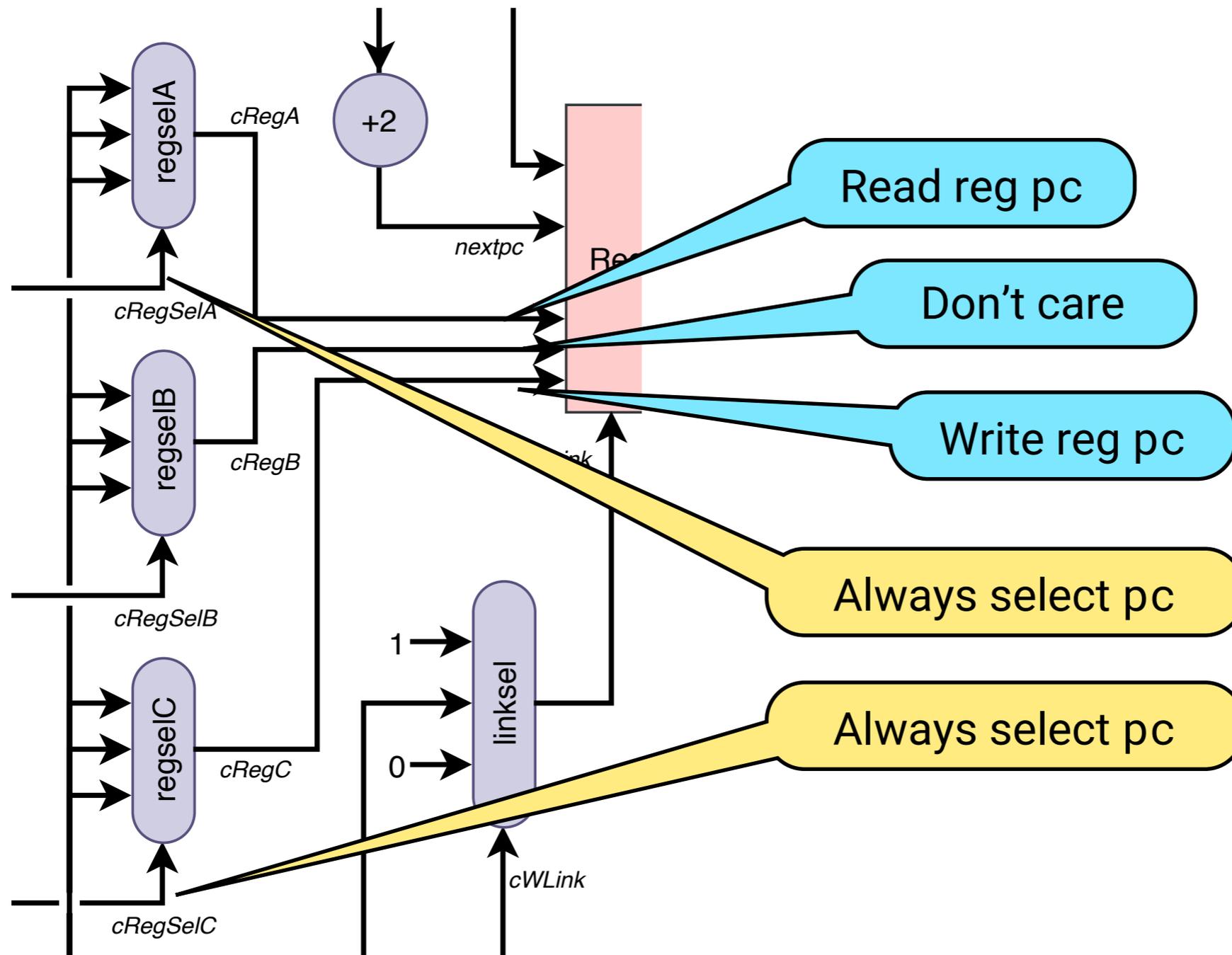


Rules 26–27 of 0 ... 31

	Instruction	cRegSel A/B/C	cRand2	cShiftOp/ Amt	cAlu Sel	cMem Rd/Wr	cWFlags/ Reg/Link
18: 19:	b<cond>	Rpc / _ / Rpc					

- Always select pc as the first register to be read, and the register to be (conditionally) written.

Feeding the ALU

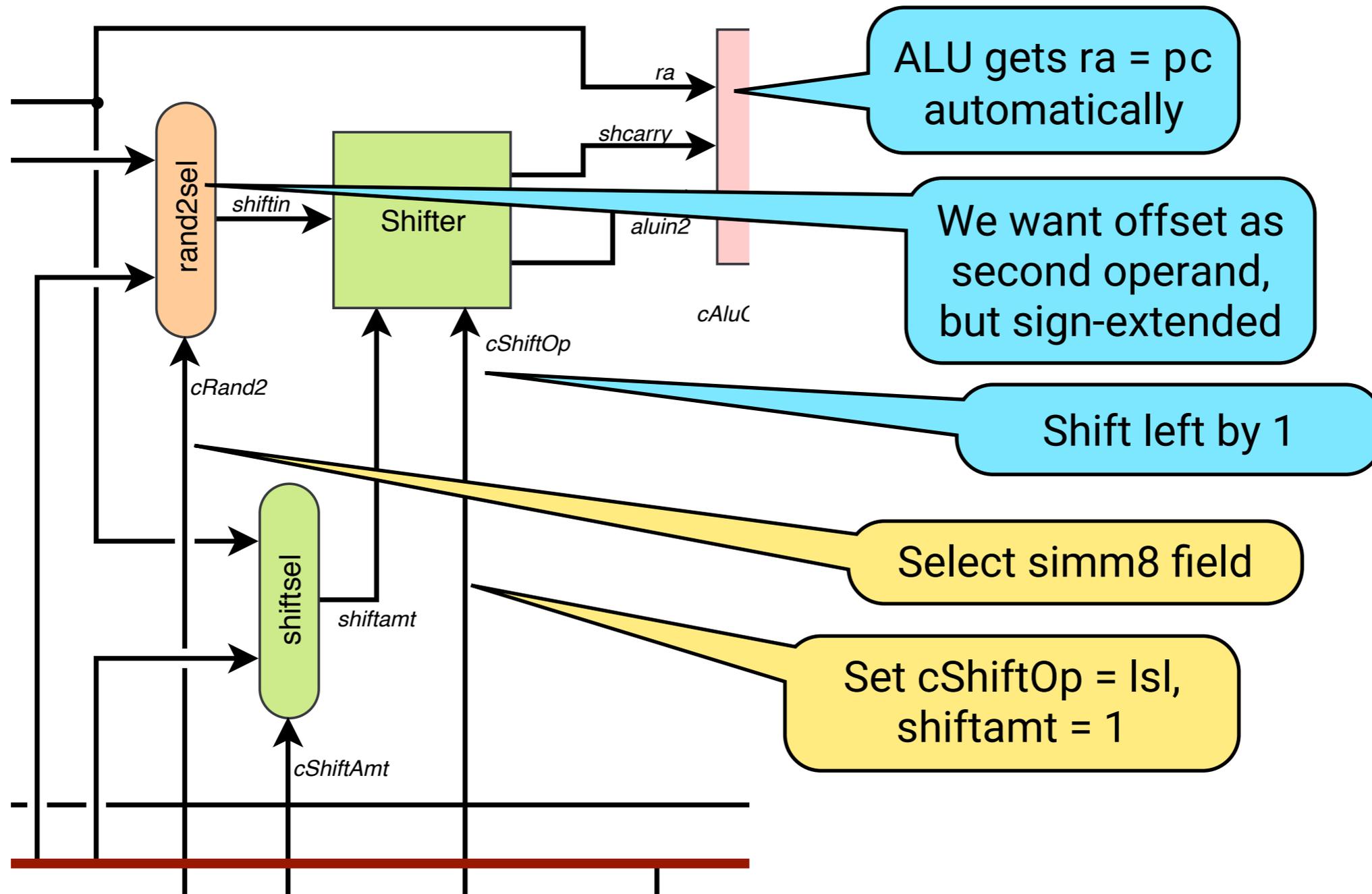


In the control word

	Instruction	cRegSel A/B/C	cRand2	cShiftOp/ Amt	cAlu Sel	cMem Rd/Wr	cWFlags/ Reg/Link
18: 19:	b<cond>	Rpc/_/Rpc	Simm8	Ls1/Sh1			

- Select immediate field as second operand, with sign-extension.
- Scale by 2, shifting left by 1 place.

Performing the operation

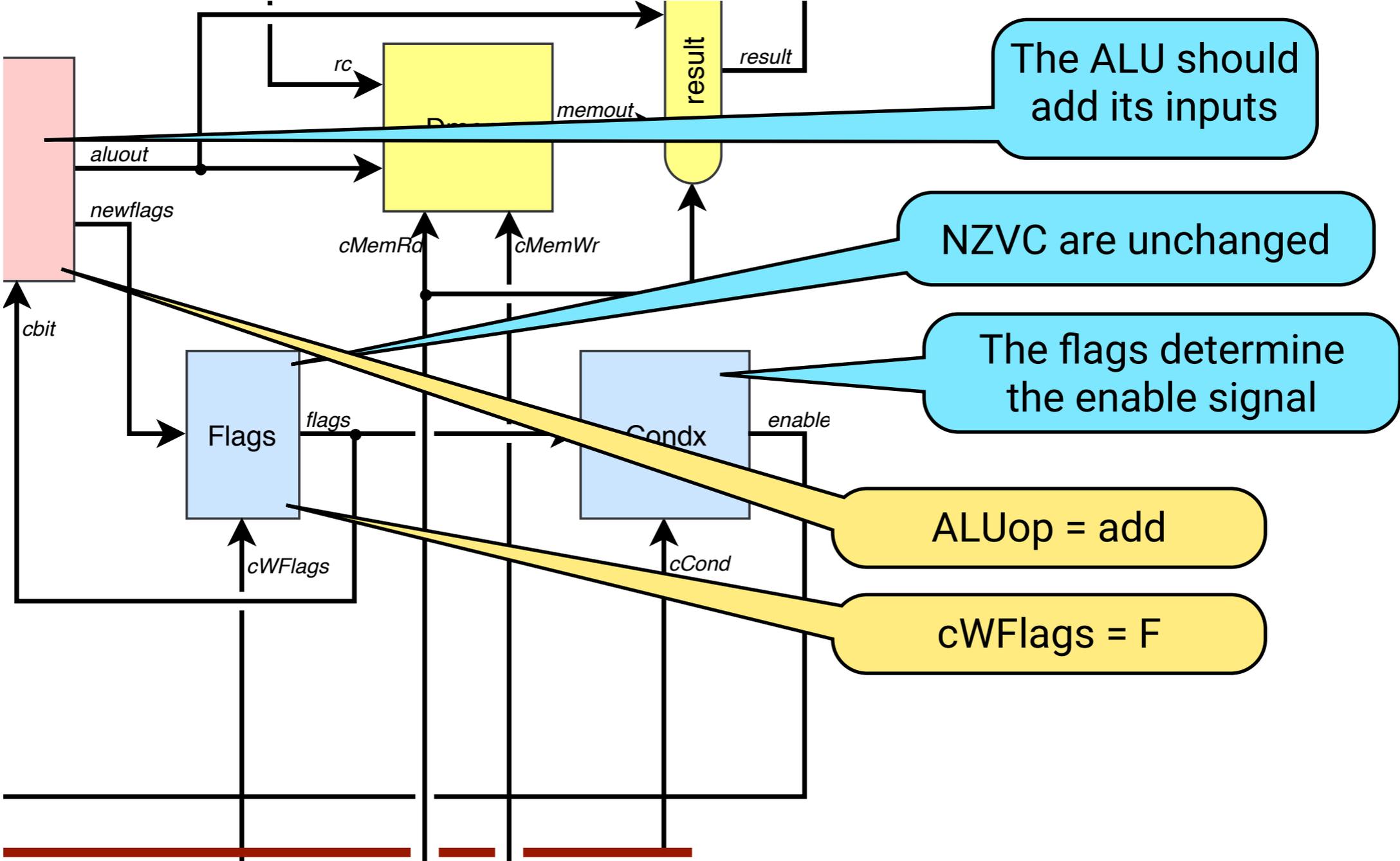


In the control word

	Instruction	cRegSel A/B/C	cRand2	cShiftOp/ Amt	cAlu Sel	cMem Rd/Wr	cWFlags/ Reg/Link
18: 19:	b<cond>	Rpc/_/Rpc	Simm8	Ls1/Sh1	Add	F/F	F/ /

- The ALU adds $pc+4$ and the scaled and sign-extended offset.
- No memory transaction needed.
- The flags are used but not changed.

Conditional execution

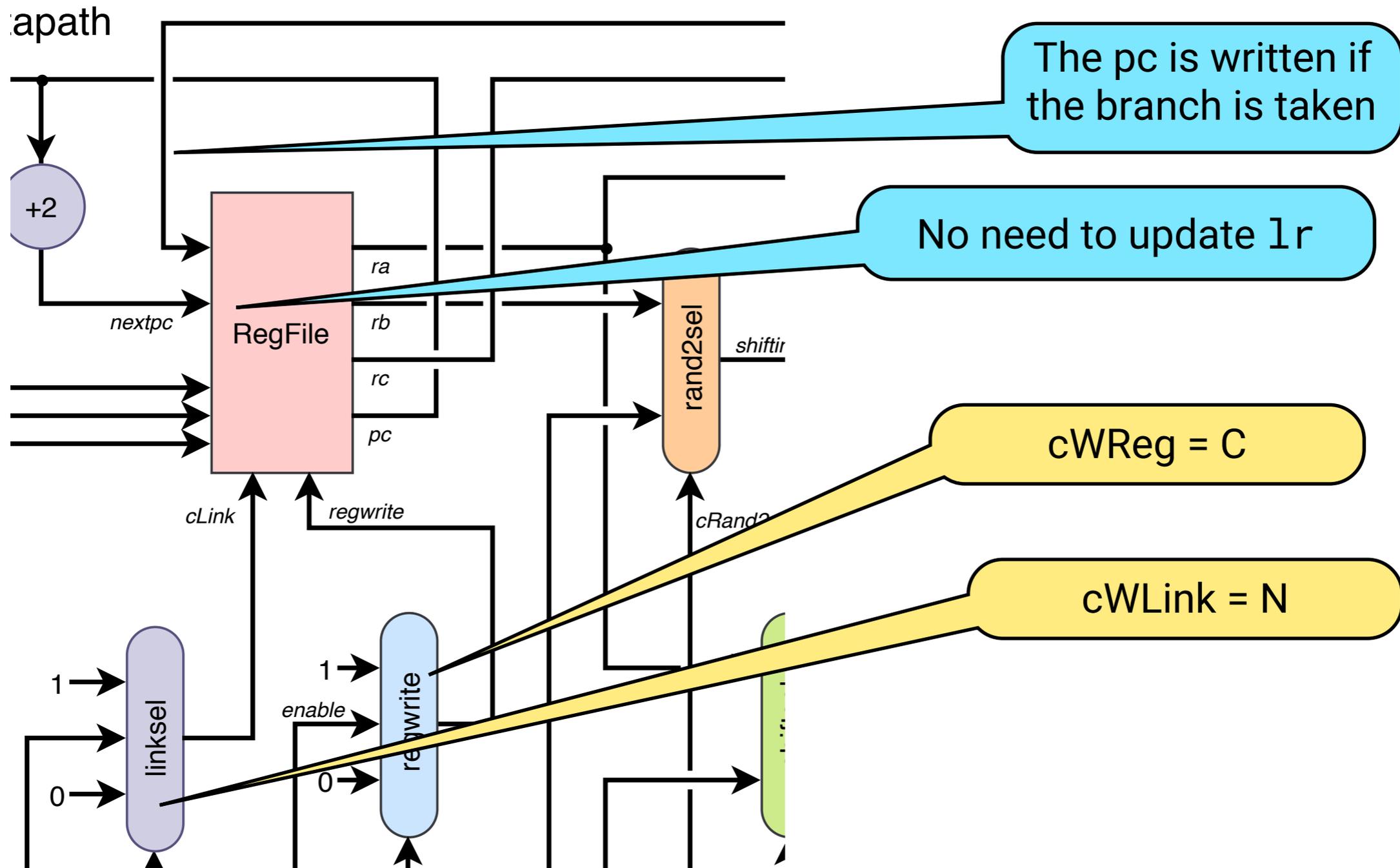

In the control word

	Instruction	cRegSel A/B/C	cRand2	cShiftOp/ Amt	cAlu Sel	cMem Rd/Wr	cWFlags/ Reg/Link
18: 19:	b<cond>	Rpc/_/Rpc	Simm8	Ls1/Sh1	Add	F/F	F/ C / N

- The branch target is always computed.
- It is written into the pc if the enable signal is true.
- There's no need to update the 1r register.