

Designing a datapath

Digital Systems – Lecture 21



UNIVERSITY OF
OXFORD

Department of
**COMPUTER
SCIENCE**

In this part

Stage-by-stage development of a *single-cycle* datapath able to execute many Thumb instructions.


- We won't have pipelined fetch and decode – so the clock speed will be limited.
- We won't implement the control needed for multi-cycle instructions like push and pop.
- And no interrupts, either.

In this lecture

Stage-by-stage development of a datapath design:

- Fetching and decoding
- Arithmetic between registers
- Immediate operands
- Load and store instructions
- Shifts


The complete datapath

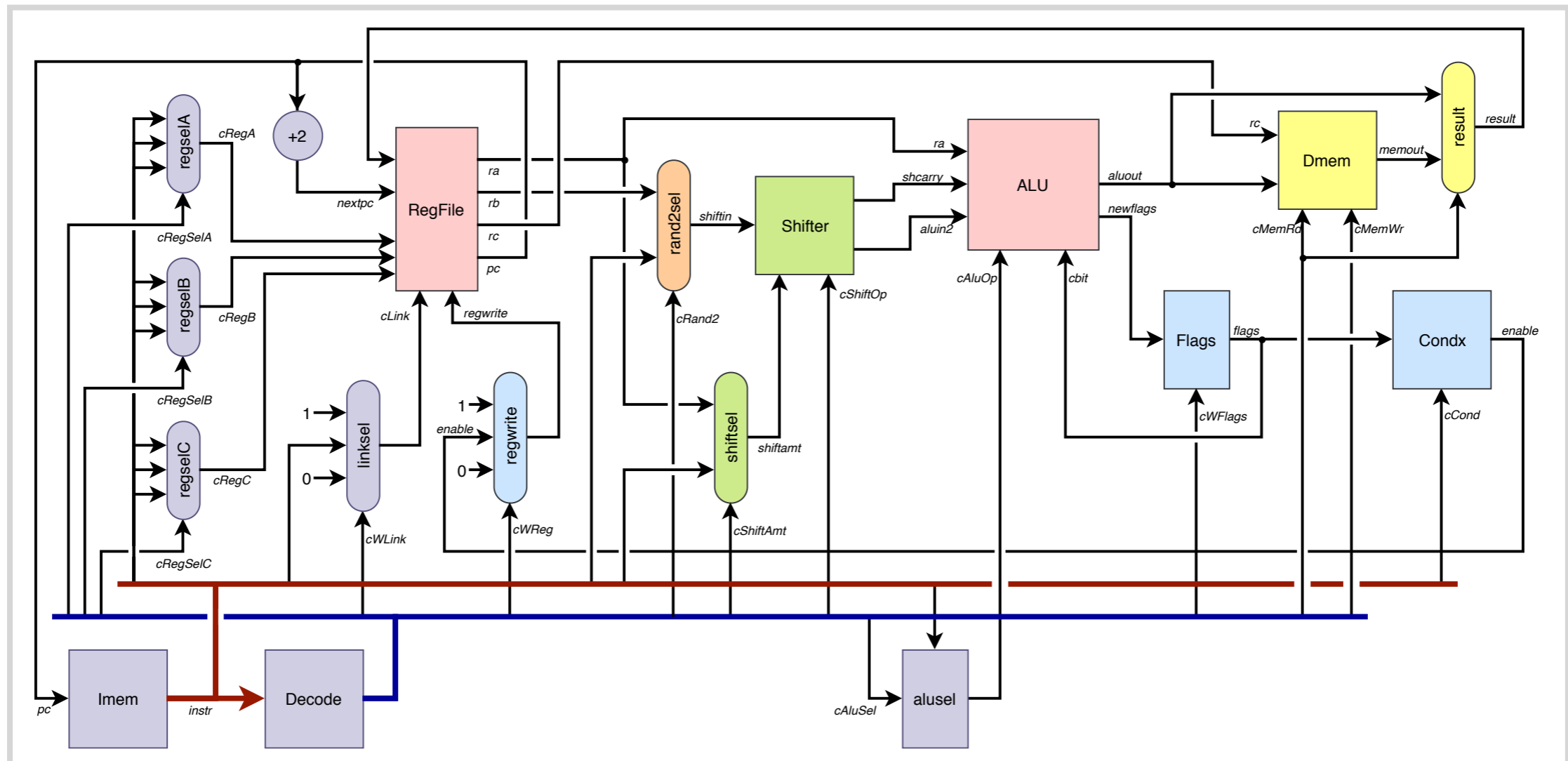

Stage 1: Instruction fetch




Stage 1: Instruction fetch

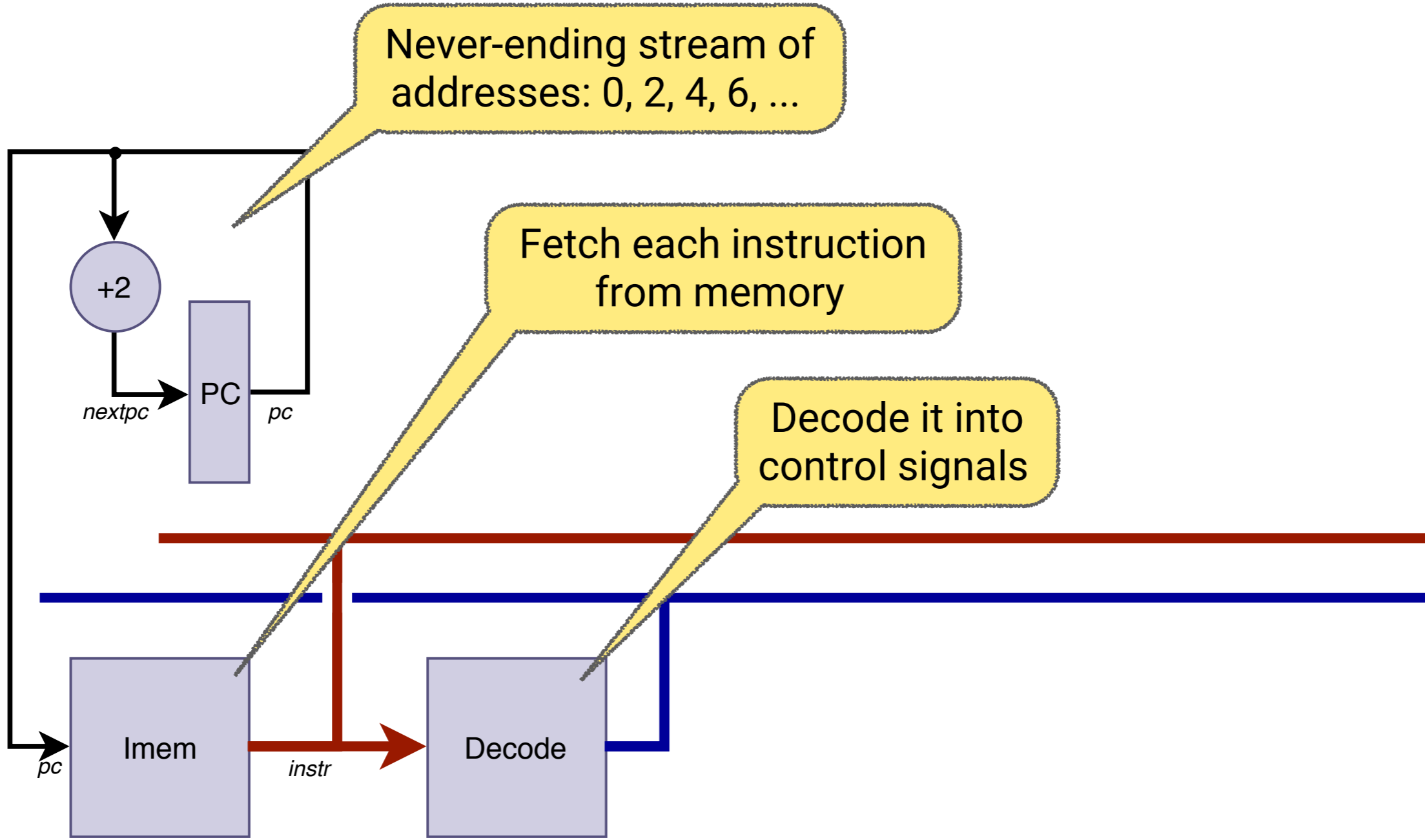

Stage 1: Instruction fetch




Stage 2: ALU operations

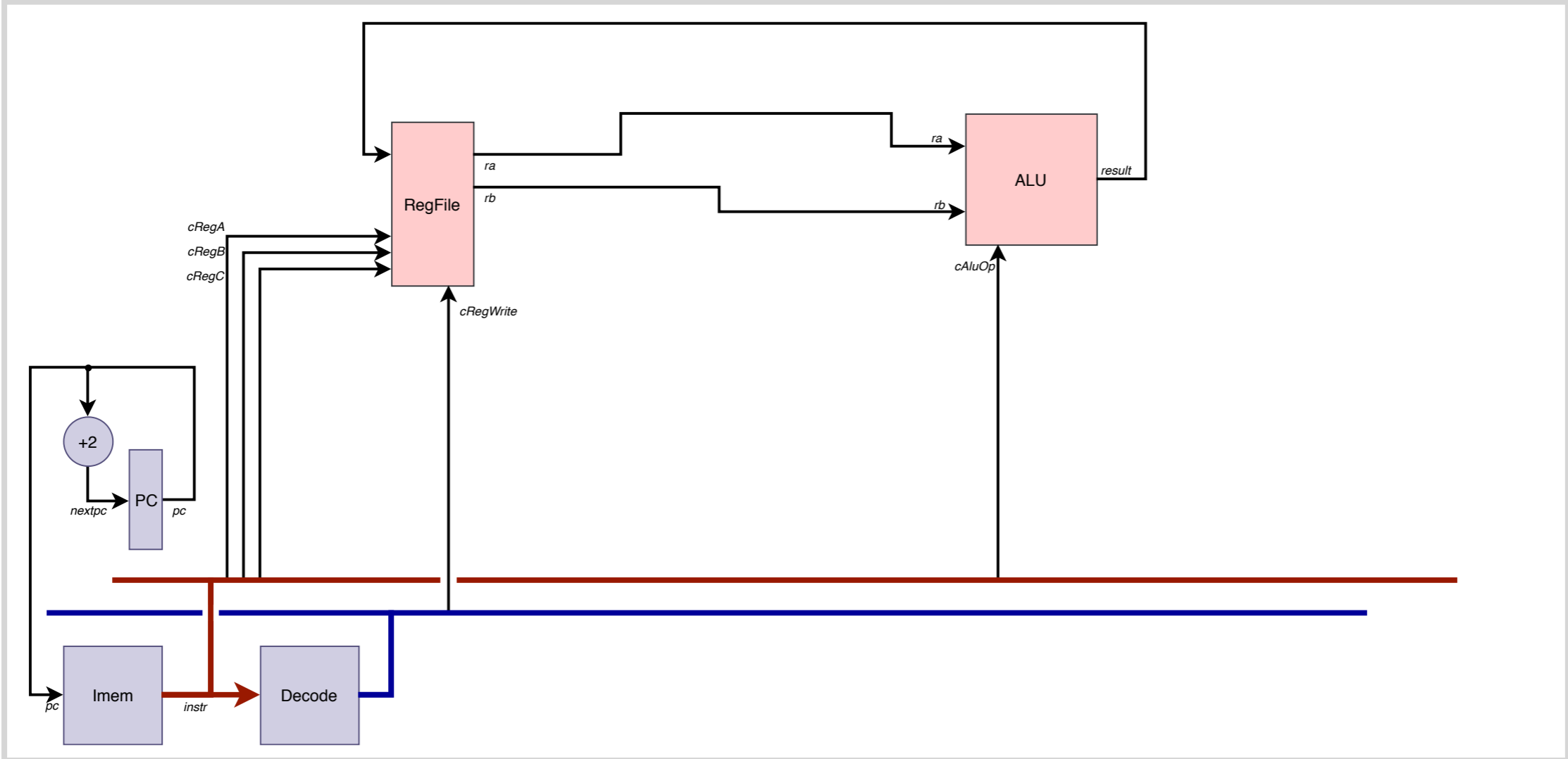

adds <Rx>, <Ry>, <Rz>

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	0	0	1	1	0	0	Rz			Ry			Rx		

Stage 2: ALU operations

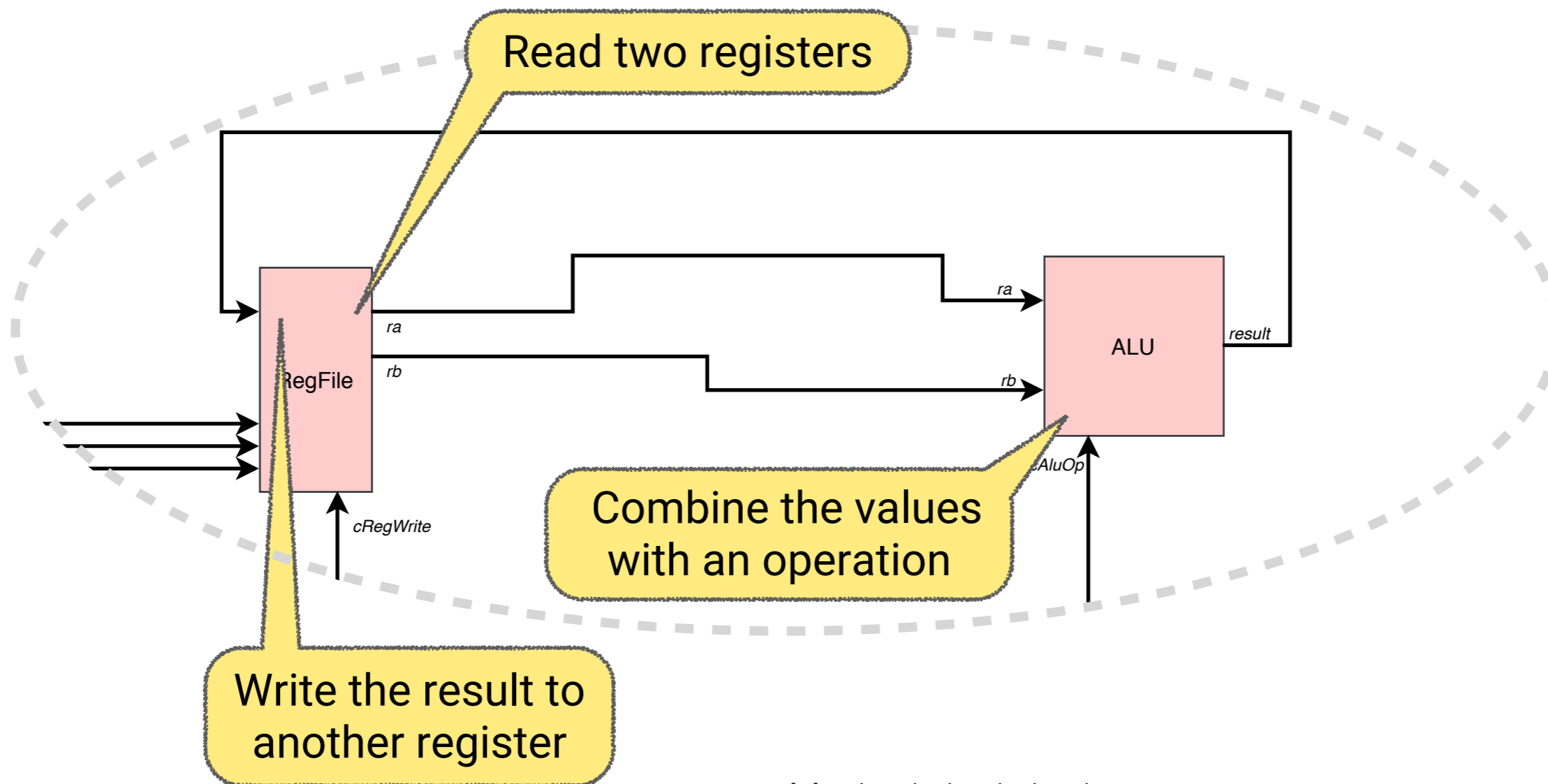

adds $\langle Rx \rangle, \langle Ry \rangle, \langle Rz \rangle$

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	0	0	1	1	0	0	Rz			Ry			Rx		

Reg-to-reg operations

adds $\langle Rx \rangle, \langle Ry \rangle, \langle Rz \rangle$

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	0	0	1	1	0	0	Rz		Ry		Rx				


subs $\langle Rx \rangle, \langle Ry \rangle, \langle Rz \rangle$

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	0	0	1	1	0	1	Rz		Ry		Rx				


ands $\langle Rx \rangle, \langle Ry \rangle$

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	1	0	0	0	0	0	0	0	0	Ry		Rx			

Stage 2: ALU operations

 


Stage 3: Immediate operands

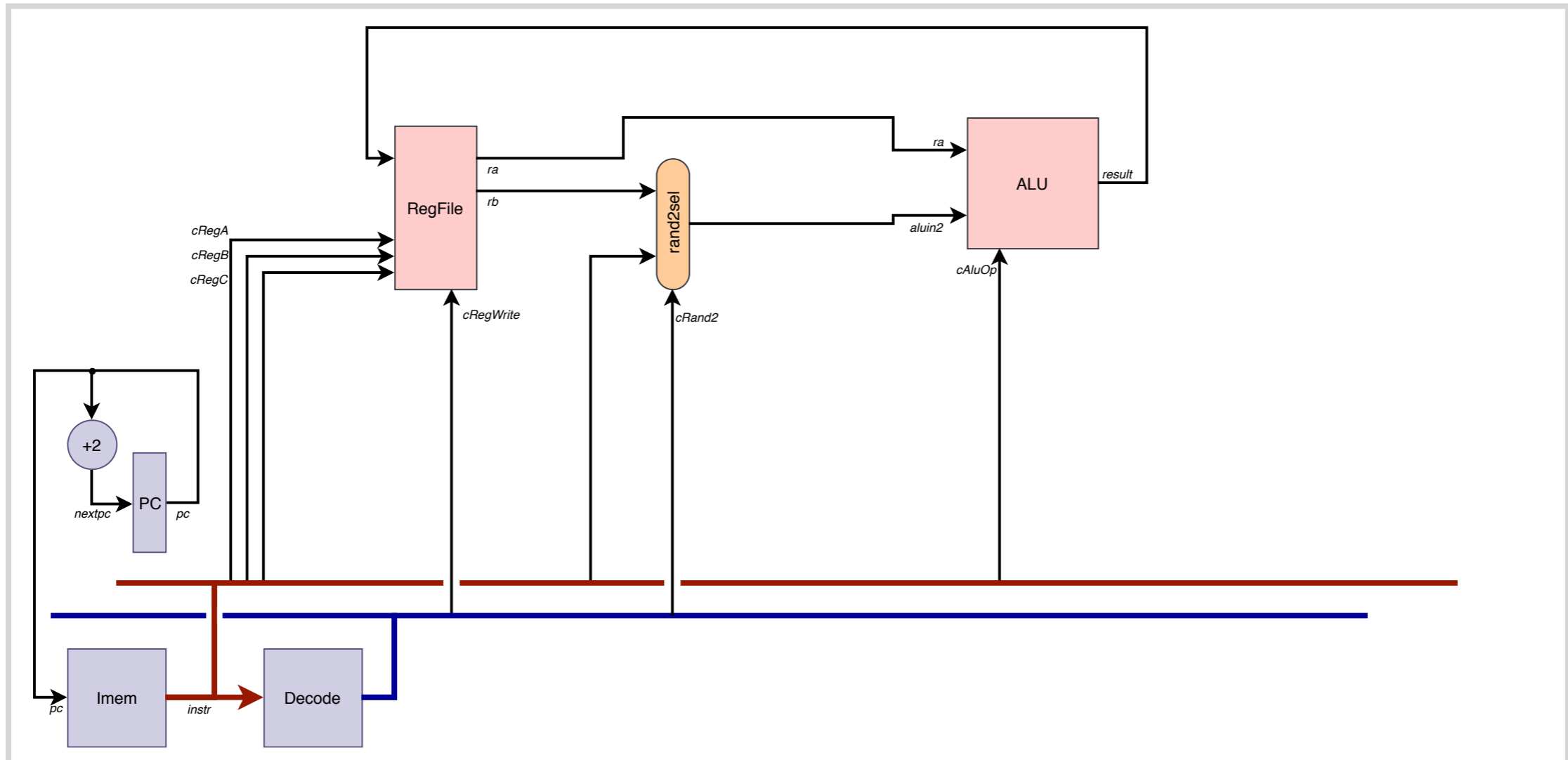

adds <Rx>,<Ry>,<imm3>

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	0	0	1	1	1	0	imm3			Ry			Rx		

Stage 3: Immediate operands

 


adds <Rx>,<Ry>,<imm3>


15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	0	0	1	1	1	0	imm3			Ry			Rx		

Operations with immediate field


adds <Rx>,<Ry>,<imm3>

 

adds <Rw>,<imm8>

 


movs <Rw>,<imm8>

 


Control signals

Instruction	cRand2	cAluOp	cRegWrite
adds r	RegB	Add	T
adds i3	Imm3	Add	T
adds i8	Imm8	Add	T
subs r	RegB	Sub	T
subs i3	Imm3	Sub	T
subs i8	Imm8	Sub	T
ands r	RegB	And	T
movs r	RegB	Mov	T
movs i8	Imm8	Mov	T

Stage 3: Immediate operands

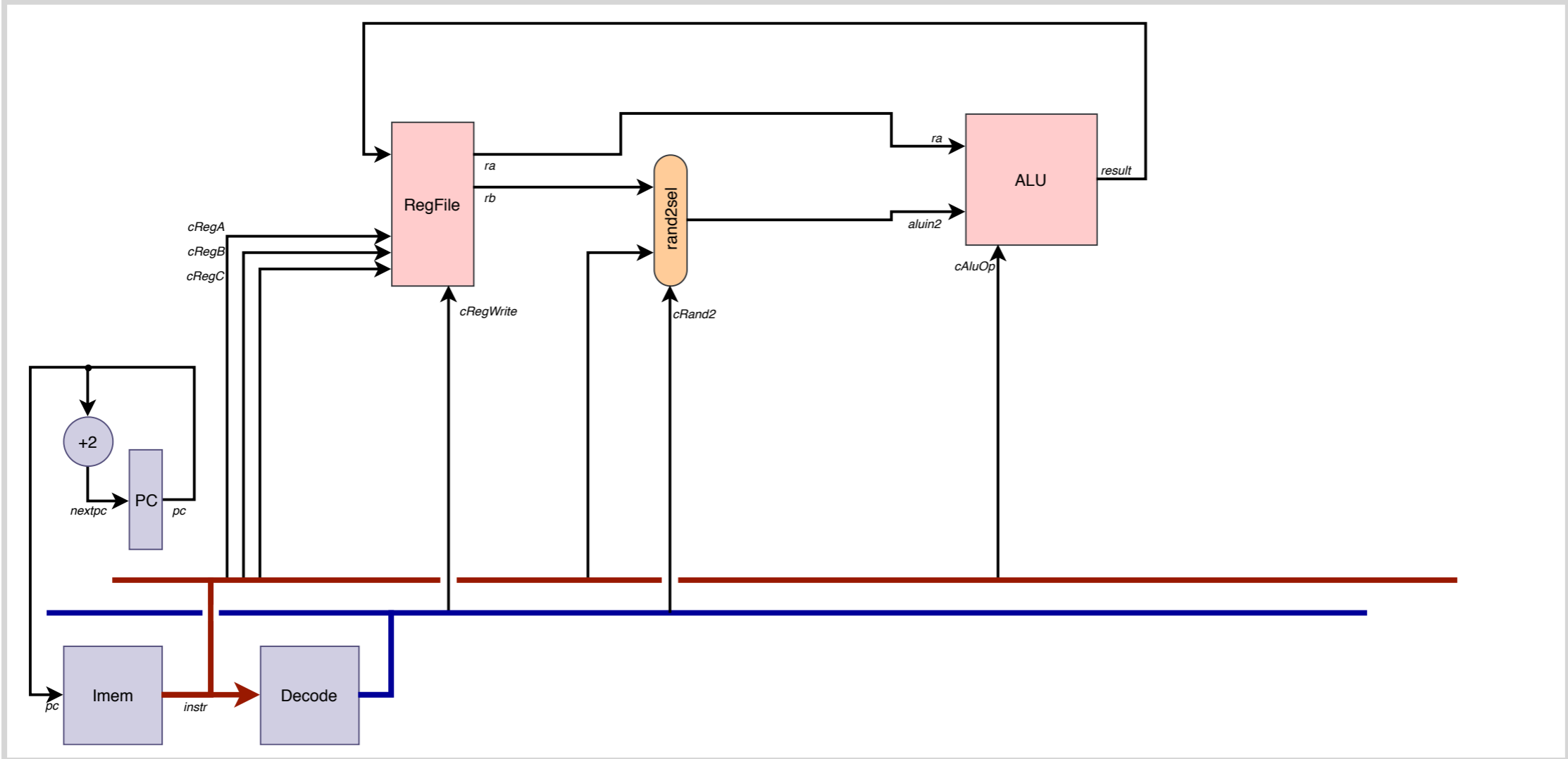


Stage 4: Data memory

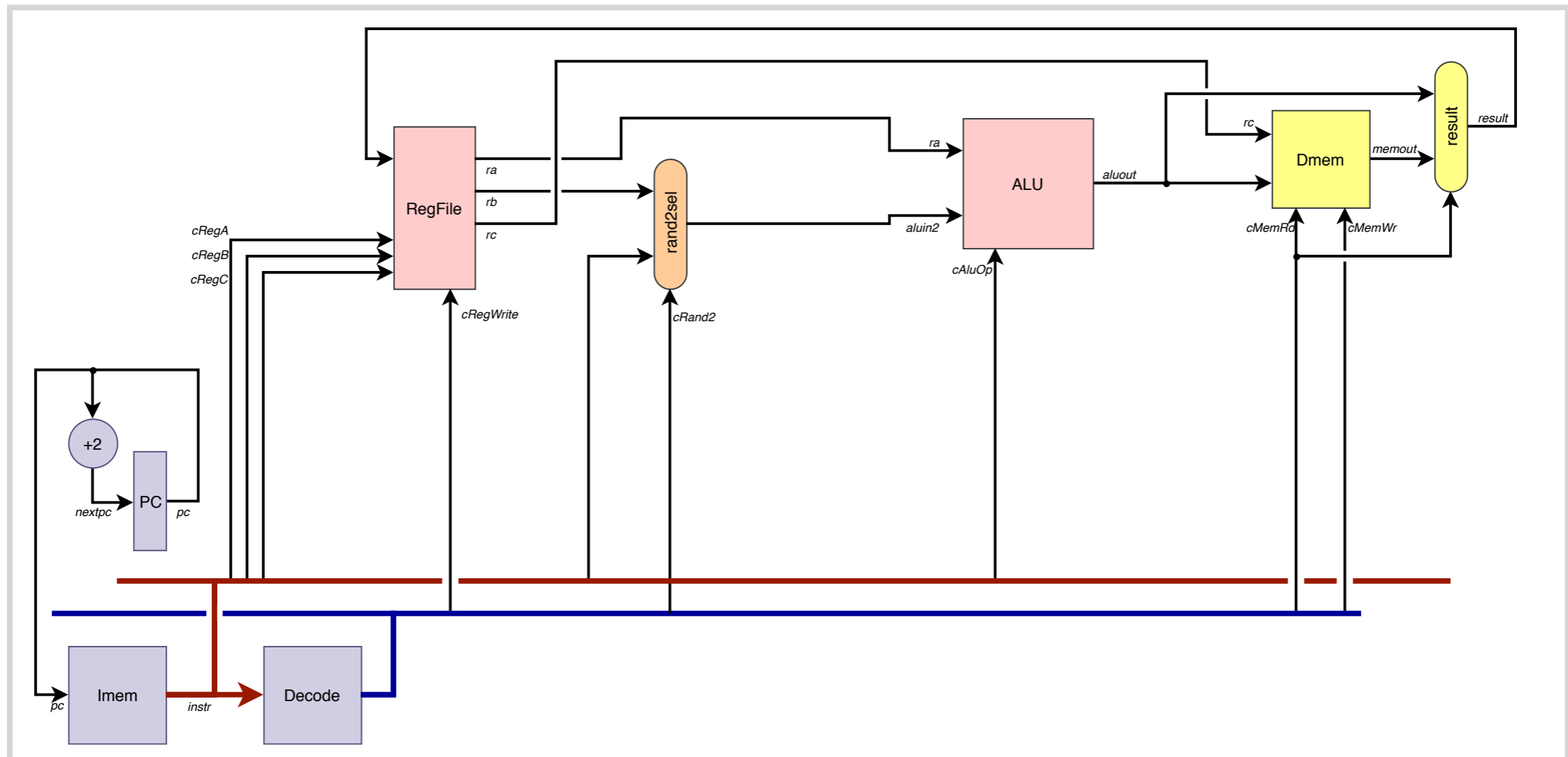

ldr <Rx>,[<Ry>,<Rz>]

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	1	0	1	1	0	0	Rz			Ry			Rx		

Stage 4: Data memory

 


ldr <Rx>,[<Ry>,<Rz>]


15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	1	0	1	1	0	0	Rz			Ry			Rx		

Load and store instructions

ldr <Rx>,[<Ry>,<Rz>]

 


str <Rx>,[<Ry>,<Rz>]

 

Instruction	cRand2	cAluOp	cMemRd	cMemWr	cRegWrite
adds r	RegB	Add	F	F	T
movs i8	Imm8	Mov	F	F	T
ldr r	RegB	Add	T	F	T
str r	RegB	Add	F	T	F



Stage 5: Barrel shifter

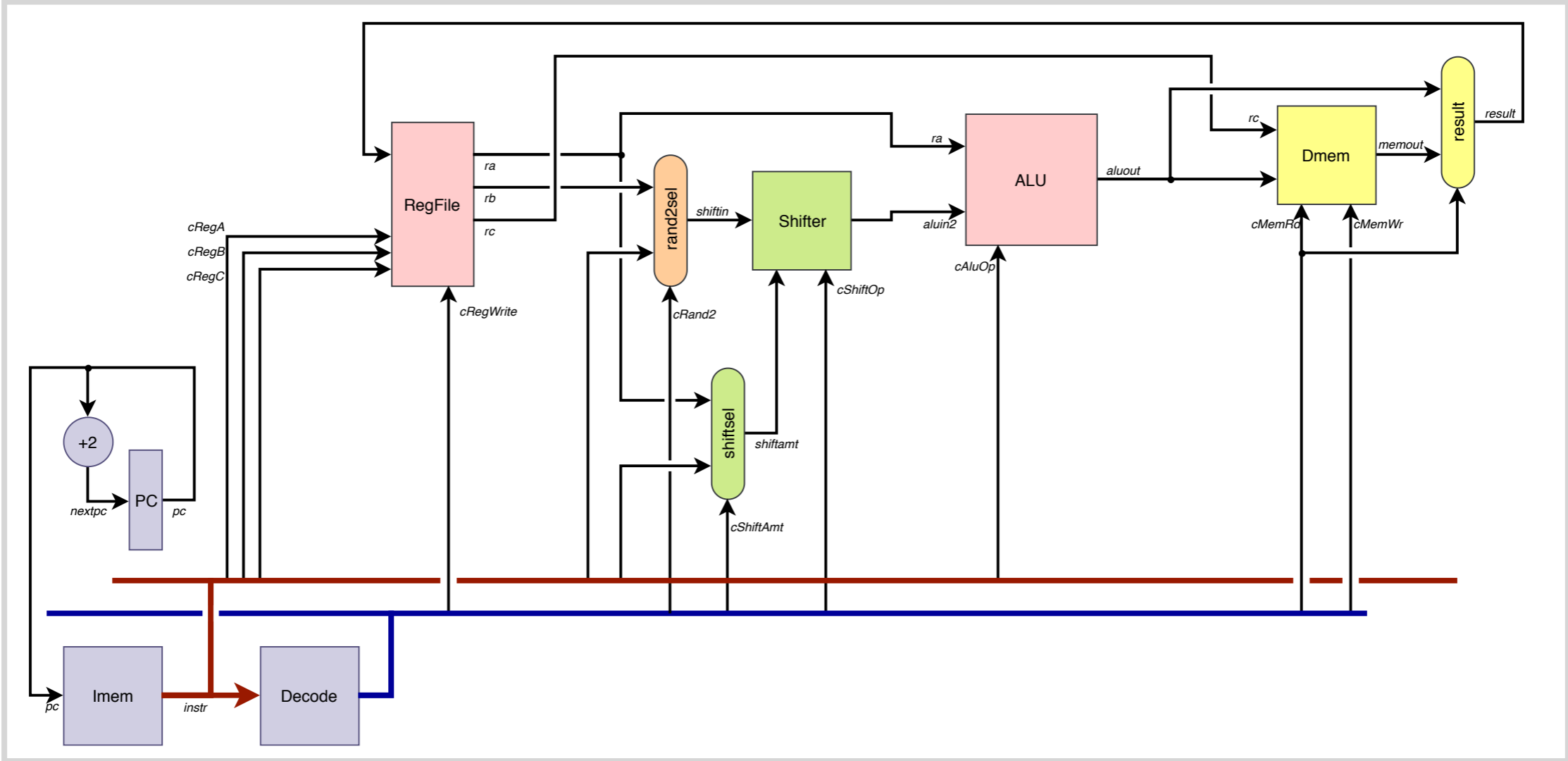

lsls <Rx>, <Ry>, #<imm5>

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	0	0	0	0	imm5					Ry			Rx		

Stage 5: Barrel shifter

 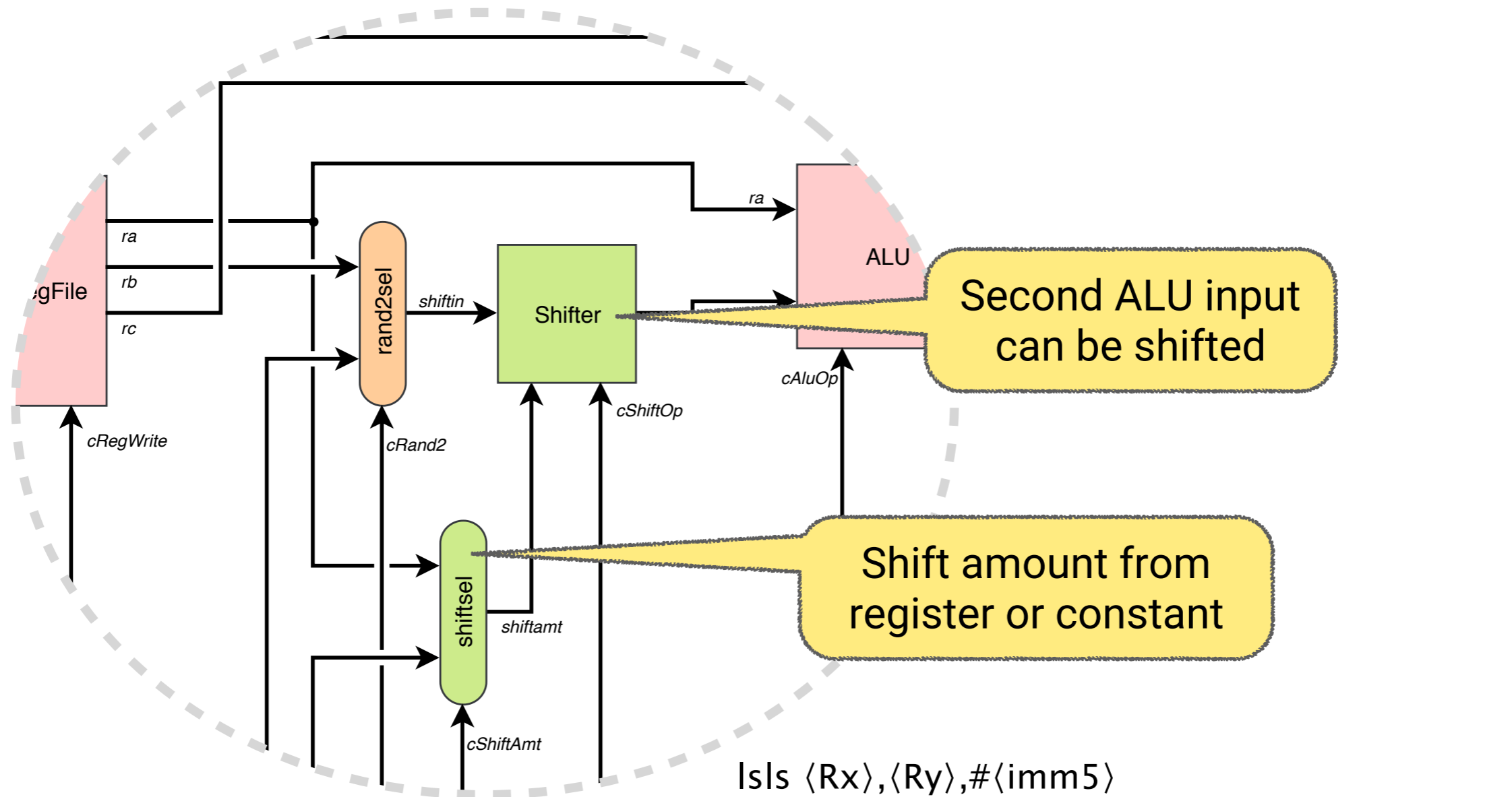

Shifts and immediate load/stores

lsls $\langle Rx \rangle, \langle Ry \rangle, \# \langle imm5 \rangle$

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	0	0	0	0	imm5					Ry		Rx			

rors $\langle Rx \rangle, \langle Ry \rangle$

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	1	0	0	0	0	0	0	1	1	1	Ry		Rx		

ldr $\langle Rx \rangle, [\langle Ry \rangle, \# \langle imm5 \rangle]$

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	1	1	0	1	imm5					Ry		Rx			

str $\langle Rx \rangle, [\langle Ry \rangle, \# \langle imm5 \rangle]$

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	1	1	0	0	imm5					Ry		Rx			

Updated control signals

Instruction	cRand2	cShiftOp	cShiftAmt	cAluOp	cMemRd/Wr	cRegWrite
adds r	RegB	Ls1	Sh0	Add	F/F	T
movs i8	Imm8	Ls1	Sh0	Mov	F/F	T
ldr r	RegB	Ls1	Sh0	Add	T/F	T
str r	RegB	Ls1	Sh0	Add	F/T	F
lsls i5	RegB	Ls1	ShImm	Mov	F/F	T
rors r	RegB	Ror	ShReg	Mov	F/F	T
ldr i5	Imm5	Ls1	Sh2	Add	T/F	T
str i5	Imm5	Ls1	Sh2	Add	F/T	F

The story so far

