

---

# Digital Hardware: Carry Lookahead Adder

Mike Spivey, Hilary Term 2004

## 1 $2^k$ -input AND gate

Let's begin with two easier circuits. To build an AND gate with  $2^k$  inputs from 2-input gates, the best plan is to use a tree of gates as shown in the diagram (Figure 1). We can describe this circuit by a purely functional program:

```
annd :: [Bool] → Bool
annd [x] = x
annd xs =
  annd (take (n/2) xs) ∧ annd (drop (n/2) xs)
  where n = length xs
```

Alternatively, we could replace the second equation with

```
annd xs = annd (zipWith (∧) (evens xs) (odds xs))
```

 


Figure 1: A tree of AND gates

## 2 Digital Hardware: Carry Lookahead Adder

which describes the tree ‘bottom-up’ instead of ‘top-down’.

Although these are recursive functional programs, if we fix the length of the input list, we can unwind the recursion and get a flat expression for the result – effectively a circuit:

$$\begin{aligned} & \mathit{annd} [x_0, x_1, x_2, x_3, x_4, x_5, x_6, x_7] \\ &= \mathit{annd} [x_0 \wedge x_1, x_2 \wedge x_3, x_4 \wedge x_5, x_6 \wedge x_7] \\ &= \mathit{annd} [(x_0 \wedge x_1) \wedge (x_2 \wedge x_3), (x_4 \wedge x_5) \wedge (x_6 \wedge x_7)] \\ &= \mathit{annd} [((x_0 \wedge x_1) \wedge (x_2 \wedge x_3)) \wedge ((x_4 \wedge x_5) \wedge (x_6 \wedge x_7))] \\ &= ((x_0 \wedge x_1) \wedge (x_2 \wedge x_3)) \wedge ((x_4 \wedge x_5) \wedge (x_6 \wedge x_7)) \end{aligned}$$

## 2 $2^k$ -bit comparator

Let’s design a circuit that takes two binary numbers of  $2^k$  bits each and computes one of the values  $Lt$ ,  $Eq$ ,  $Gt$  to indicate the result of comparing them:

$$\mathit{compare} :: [\mathit{Bit}] \rightarrow [\mathit{Bit}] \rightarrow \mathit{LEG}$$

where

$$\mathbf{data} \mathit{LEG} = \mathit{Lt} \mid \mathit{Eq} \mid \mathit{Gt}$$

We’ll decide later how to represent  $\mathit{LEG}$  values as bits. Obviously,

$$\mathit{compare} [] [] = \mathit{Eq}$$

Also (remembering that we represent numbers LSB first)

$$\begin{aligned} \mathit{compare} (as ++ [a]) (bs ++ [b]) = \\ & \mathbf{if} \ a < b \ \mathbf{then} \ \mathit{Lt} \\ & \mathbf{else\ if} \ a > b \ \mathbf{then} \ \mathit{Gt} \\ & \mathbf{else} \ \mathit{compare} \ as \ bs \end{aligned}$$

Let’s define a function  $\mathit{cf}$  and an operator  $\odot$  by

$$\begin{aligned} \mathit{cf} &:: \mathit{Bit} \rightarrow \mathit{Bit} \rightarrow \mathit{LEG} \\ \mathit{cf} \ 0 \ 0 &= \mathit{Eq}; \ \mathit{cf} \ 0 \ 1 = \mathit{Lt}; \ \mathit{cf} \ 1 \ 0 = \mathit{Gt}; \ \mathit{cf} \ 1 \ 1 = \mathit{Eq} \\ (\odot) &:: \mathit{LEG} \rightarrow \mathit{LEG} \rightarrow \mathit{LEG} \\ z \odot \mathit{Lt} &= \mathit{Lt} \\ z \odot \mathit{Eq} &= z \\ z \odot \mathit{Gt} &= \mathit{Gt} \end{aligned}$$

The we find

$$\begin{aligned} \mathit{compare} (as ++ [a]) (bs ++ [b]) \\ = \mathit{compare} \ as \ bs \odot \ \mathit{cf} \ a \ b \end{aligned}$$

This makes  $\mathit{compare}$  fit into a well-known pattern of recursion:

$$\mathit{compare} \ as \ bs = \mathit{foldl} (\odot) \ \mathit{Eq} (\mathit{zipWith} \ \mathit{cf} \ as \ bs)$$

But  $\mathit{dot}$  is associative, so we can play the same trick as with AND:

$$\mathit{compare} \ as \ bs = \mathit{pfold} (\odot) (\mathit{zipWith} \ \mathit{cf} \ as \ bs)$$

where

$$\begin{aligned} \mathit{pfold} (\oplus) [x] &= x \\ \mathit{pfold} (\oplus) xs &= \\ & \mathit{pfold} (\oplus) (\mathit{zipWith} (\oplus) (\mathit{evens} \ xs) (\mathit{odds} \ xs)) \end{aligned}$$

 


Figure 2: Karnaugh maps for p and q

This comparison circuit has size  $O(2^k)$  but depth  $O(k)$ , because the comparison indicators are combined by a binary tree of depth  $n$ .

If we represent  $Lt$ ,  $Eq$ ,  $Gt$  by the bit patterns (0, 1), (0, 0), (1, 0), then the  $cf$  function becomes  $cf\ a\ b = (a \wedge \neg b, b \wedge \neg a)$ . And if  $(p, q) = (u, v) \oplus (w, x)$ , then we get the Karnaugh maps for  $p$  and  $q$  shown in Figure 2:<sup>1</sup> From these maps we read off  $p = w \vee (\neg x \wedge u)$  and  $q = x \vee (\neg w \wedge v)$ .

### 3 Carry-lookahead adder

Now, at last, we can look at the carry-lookahead adder. We start from the ripple-carry adder:

$$adder\ as\ bs = ripple\ fulladd\ 0\ (zip\ as\ bs)$$

where  $fulladd :: Bit \rightarrow (Bit, Bit) \rightarrow (Bit, Bit)$  models a full adder, and

$$ripple :: (\alpha \rightarrow \beta \rightarrow (y, \alpha)) \rightarrow \alpha \rightarrow [\beta] \rightarrow [y]$$

is defined so that

$$ripple\ f\ c_0\ [x_0, x_1, \dots, x_{n-1}] = [y_0, y_1, \dots, y_{n-1}]$$

where

$$(y_0, c_1) = f\ c_0\ x_0$$

$$(y_1, c_2) = f\ c_1\ x_1$$

...

$$(y_{n-1}, c_n) = f\ c_{n-1}\ x_n$$

Now let's concentrate on the carry bits:

<sup>1</sup> In the Karnaugh maps, I've marked with an X those entries that we don't care about, because the inputs  $(u, v) = (1, 1)$  or  $(w, x) = (1, 1)$  can never occur. The circuit will work properly whatever output the  $\odot$  box produces for these inputs, so we are free to choose each X as 0 or 1, whichever gives the fewest, largest rectangles in the Karnaugh map.

#### 4 Digital Hardware: Carry Lookahead Adder

$fulladd\ c\ (0, 0) = (?, 0)$   
 $fulladd\ c\ (0, 1) = (?, c)$   
 $fulladd\ c\ (1, 0) = (?, c)$   
 $fulladd\ c\ (1, 1) = (?, 1)$

So the carry bit that is output by the full adder is one of these three things: always 0, the same as the carry input  $c$ , or always 1, depending on the two input bits  $(a, b)$ . Let's call these three possibilities kill ( $K$ ), propagate ( $P$ ) and generate ( $G$ ).

We can define a function  $kpg$  that returns these three values as appropriate:

**data**  $KPG = K \mid P \mid G$

$kpg :: (Bit, Bit) \rightarrow KPG$

$kpg\ (0, 0) = K; kpg\ (0, 1) = P; kpg\ (1, 0) = P; kpg\ (1, 1) = G$

Now let's agree to replace the carry input and output of each full adder by either  $K$  (if it was 0 before) or  $G$  (if it was 1). This gives us a new version of the full adder:

$kpg\_add :: KPG \rightarrow (Bit, Bit) \rightarrow (Bit, KPG)$

$kpg\_add\ w\ (a, b) = (sumbit\ w\ (a, b), w \otimes kpg\ (a, b))$

Where  $sumbit :: KPG \rightarrow (Bit, Bit) \rightarrow Bit$  is an appropriate function, and  $\otimes$  is the binary operation defined by

$(\otimes) :: KPG \rightarrow KPG \rightarrow KPG$

$z \otimes K = K$

$z \otimes P = z$

$z \otimes G = G$

This gives us a new version of the ripple-carry adder:

$rip\_kpg\ as\ bs = ripple\ kpg\_add\ K\ (zip\ as\ bs)$

We have not yet made any improvement - the depth of this circuit is still  $O(n)$  for adding  $n$ -bit numbers. But now we calculate as follows:

$rip\_kpg\ [a_0, \dots, a_{n-1}]\ [b_0, \dots, b_{n-1}] = [s_0, \dots, s_{n-1}]$

**where**

$(s_0, w_1) = kpg\_add\ K\ (a_0, b_0)$

$(s_1, w_2) = kpg\_add\ w_1\ (a_1, b_1)$

...

$(s_{n-1}, w_n) = kpg\_add\ w_{n-1}\ (a_{n-1}, b_{n-1})$

So for each  $i$ ,

$(s_i, w_{i+1}) = kpg\_add\ w_i\ (a_i, b_i)$

$= (sumbit\ w_i\ (a_i, b_i), w_i \otimes kpg\ (a_{i-1}, b_{i-1}))$

Thus

$[s_0, \dots, s_{n-1}]$

$= zipWith\ sumbit\ [w_0, \dots, w_{n-1}]\ [(a_0, b_0), \dots, (a_{n-1}, b_{n-1})]$

with  $w_0 = K$  and  $w_{i+1} = w_i \otimes kpg(a_i, b_i)$ . We see that  $w_i = K \otimes kpg(a_0, b_0) \otimes \dots \otimes kpg(a_{i-1}, b_{i-1})$ . This gives us a new adder:

```

cla as bs =
  zipWith sumbit carries inputs
  where
    carries = par_prefix (⊗) K (map kpg inputs)
    inputs = zip as bs

```

This uses a function *par\_prefix*, defined so that

```

par_prefix (%) a [x0, ..., xn-1]
  = [a, a % x0, a % x0 % x1, ..., a % x0 % ... % xn-2]

```

Now for the really clever bit: we can define *par\_prefix* in such a way that the  $n$  results can be evaluated in parallel, provided  $\%$  is associative and  $n$  is a power of 2. Observe that if  $xs = [x_0, \dots, x_{2k-1}]$  then

```

par_prefix (%) a xs
  = [a, a % x0, a % x0 % x1, a % x0 % x1 % x2, ...,
     a % x0 % x1 % ... % x2k-3,
     a % x0 % x1 % ... % x2k-3 % x2k-2]
  = [y0, y0 % x1, y1, y1 % x2, ..., yk-1, yk-1 % x2k-2]

```

where

```

[y0, y1, ..., yk-1]
  = [a, a % (x0 % x1), ..., a % (x0 % x1) % ... % (x2k-4 % x2k-3)]
  = par_prefix (%) a [x0 % x1, x2 % x3, ..., x2k-4 % x2k-3]
  = par_prefix (%) a (zipWith (%) (evens xs) (odds xs))

```

So we can define *par\_prefix* as follows:

```

par_prefix (%) a [x] = [a]
par_prefix (%) a xs =
  concat (zipWith g es (par_prefix (%) a (zipWith (%) es os)))
  where
    es = evens xs; os = odds xs
    g x y = [y, y % x]

```

The size and depth of this prefix circuit satisfy

$$S(2^k) = O(2^{k-1}) + S(2^{k-1}) + O(2^{k-1}),$$

$$D(2^k) = O(1) + D(2^{k-1}) + O(1).$$

So  $S(2^k) = O(2^k)$  and  $D(2^k) = O(k)$ . The resulting adder circuit is sketched in Figure 3.

6 Digital Hardware: Carry Lookahead Adder

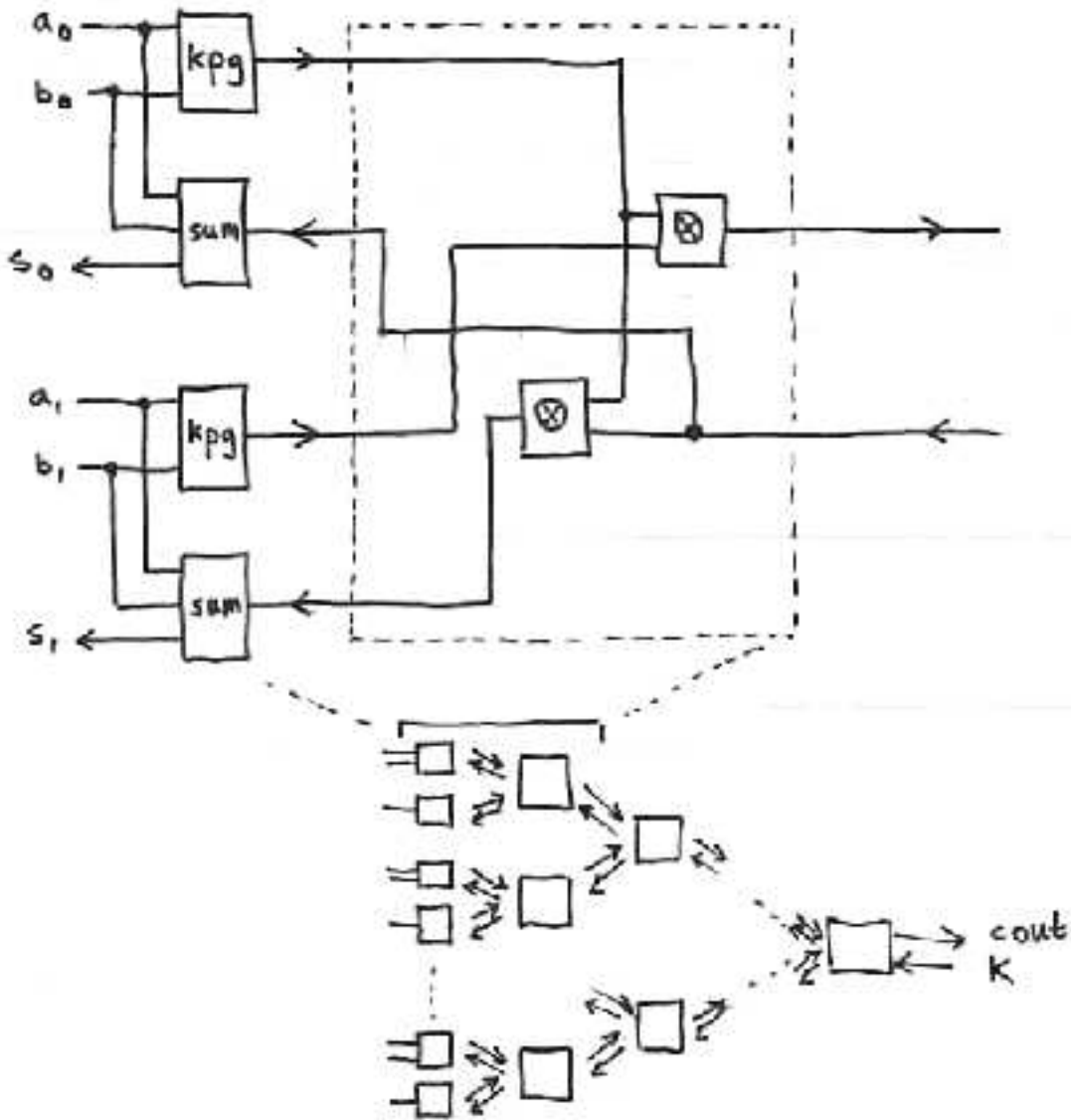


Figure 3: Carry lookahead adder